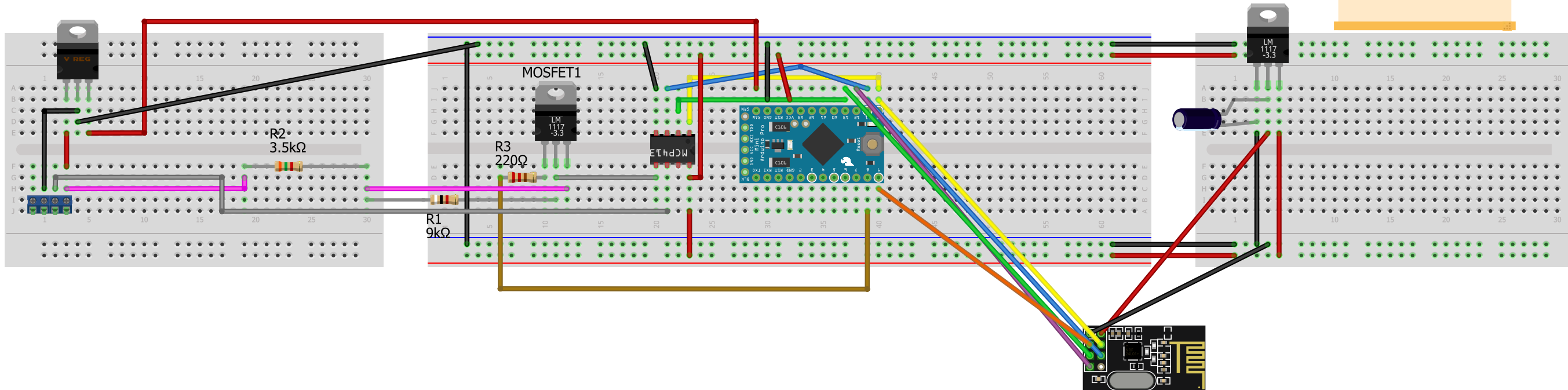


Output from this voltage regulator will go to NRF24L01+



Add a 10μF capacitor across GND and Vcc of NRF24L01+ directly to provide sufficient current required for it.